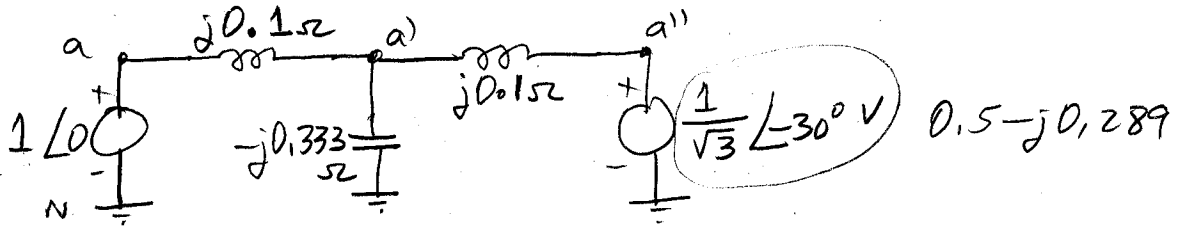


Z0.11 Balanced \rightarrow use one-line with line-to-neutral voltages

$$Z_c = \frac{Z_A}{3} = \frac{-j1}{3} = -j0,333 \Omega$$

$$V_{a''b''} = 1\angle 0^\circ, \text{ so } V_{A''N} = \frac{1}{\sqrt{3}} \angle -30^\circ$$



Use KCL at a'

$$\frac{V_{a'N} - 1\angle 0}{j0.1} + \frac{V_{a'N}}{-j0.333} + \frac{V_{a'N} - \frac{1}{\sqrt{3}} \angle -30^\circ}{j0.1} = 0$$

$$V_{a'N} \left[\frac{1}{j0.1} + \frac{1}{-j0.333} + \frac{1}{j0.1} \right] = \frac{1\angle 0}{j0.1} + \frac{\frac{1}{\sqrt{3}} \angle -30^\circ}{j0.1}$$

$$V_{a'N} [-j10 + j3.0 - j10] = \frac{10 \angle -90^\circ}{-j10} + \frac{5,77 \angle -120^\circ}{-2,89 - j5,00}$$

$$\hat{V}_{a'N} [-j17] = -2,89 - j15 = 15,28 \angle -100,9$$

$$\hat{V}_{a'N} = \frac{15,28 \angle -100,9}{17 \angle -90} = 0,899 \angle -10,9^\circ \text{ V}$$

$$0,883 + j0,170$$

$$\text{So } \hat{V}_{b'N} = \hat{V}_{a'N} \angle -120 = 0,899 \angle -130,9^\circ \text{ V}$$

$$\hat{V}_{c'N} = \hat{V}_{a'N} \angle +120 = 0,899 \angle 109,1^\circ \text{ V}$$

$$V_{a'b'} = V_{a'N} \sqrt{3} \angle 30^\circ = 1,557 \angle 19,1^\circ \text{ V}$$

Check KCL with the Arithmetic

$$\begin{array}{c} \leftarrow -1,70 + j1,117 \\ \downarrow 0,511 + j2,165 \\ \rightarrow 1,19 - j3,83 \end{array}$$

OK

$$\Sigma = 0$$