

2.15 . Let $V_N \equiv 0$. But, $V_{N'N} \neq 0$ because the system is NOT balanced,

However, KCL says $\tilde{I}_a + \tilde{I}_b + \tilde{I}_c = 0$,

Write some equations —

$$\tilde{I}_a = \frac{\tilde{E}_{aN} - \tilde{V}_{N'N}}{z}, \quad \tilde{I}_b = \frac{\tilde{E}_{bN} - \tilde{V}_{N'N}}{z}, \quad \tilde{I}_c = \frac{\tilde{E}_{cN} - \tilde{V}_{N'N}}{z}$$

$\tilde{E}_{aN}, \tilde{E}_{bN}, \tilde{E}_{cN}$ given

Add the three equations (noting that $\tilde{I}_a + \tilde{I}_b + \tilde{I}_c = 0$)

$$\frac{\tilde{E}_{aN} - \tilde{V}_{N'N}}{z} + \frac{\tilde{E}_{bN} - \tilde{V}_{N'N}}{z} + \frac{\tilde{E}_{cN} - \tilde{V}_{N'N}}{z} = 0$$

Multiplying by z , and separating terms

$$3\tilde{V}_{N'N} = \tilde{E}_{aN} + \tilde{E}_{bN} + \tilde{E}_{cN}$$

$$\tilde{V}_{N'N} = \frac{\sqrt{2}/45 + 1/-90 + 1/180}{3} = \frac{\cancel{1} + j\cancel{1} - j\cancel{1} - \cancel{1}}{3} = 0$$

Coincidence!

So, using $-\tilde{E}_{aN} + \tilde{I}_a z + \tilde{V}_{N'N} = 0$,

we get $\tilde{z} = \frac{\tilde{E}_{aN}}{\tilde{I}_a} = \frac{\sqrt{2}/45}{1/-10} = \sqrt{2}/55^\circ \text{ A}$

Then, $\tilde{I}_b = \frac{\tilde{E}_{bN} - \tilde{V}_{N'N}}{\tilde{z} = \sqrt{2}/55^\circ} = \frac{1/-90}{\sqrt{2}/55^\circ} = \frac{1}{\sqrt{2}} \angle -145^\circ \text{ A}$

$\tilde{I}_c = \frac{\tilde{E}_{cN} - \tilde{V}_{N'N}}{\tilde{z} = \sqrt{2}/55^\circ} = \frac{-1}{\sqrt{2}/55} = \frac{1}{\sqrt{2}} \angle 125^\circ \text{ A}$

2.15

$$S_{3\phi} = V_{AN} I_A^* + V_{BN} I_B^* + V_{CN} I_C^*$$

$$= (\sqrt{2} \angle 45^\circ)(1 \angle +10^\circ) + (1 \angle -90^\circ)(\frac{1}{\sqrt{2}} \angle +145^\circ)$$

$$+ (1 \angle 180^\circ)(\frac{1}{\sqrt{2}} \angle -125^\circ)$$

$$= \sqrt{2} \angle 55^\circ + \frac{1}{\sqrt{2}} \angle 55^\circ + \frac{1}{\sqrt{2}} \angle 55^\circ$$

$$= (\sqrt{2} + \frac{2}{\sqrt{2}}) \angle 55^\circ = (\sqrt{2} + \sqrt{2}) \angle 55^\circ =$$

$$2\sqrt{2} \angle 55^\circ \text{ VA}$$

$$S_{3\phi}$$

Check I^2R , I^2X

Each Z , $R = \sqrt{2} \cos(55^\circ) = 0.811 \Omega$

$X = \sqrt{2} \sin(55^\circ) = j1.159 \Omega$

$$= 2.83 \angle 55^\circ \text{ VA}$$

$$= 1.623 \text{ W} + j 2.32 \text{ VAR}$$

$$P = |I_a|^2 R + |I_b|^2 R + |I_c|^2 R$$

$$= \left[(1)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 \right] (0.811) = \left[1 + \frac{1}{2} + \frac{1}{2} \right] (0.811) = 1.622 \text{ W}$$

$$Q = \left[(1)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 \right] (1.159) = (2)(1.159) = 2.32 \text{ VAR}$$

↓ OK

↓