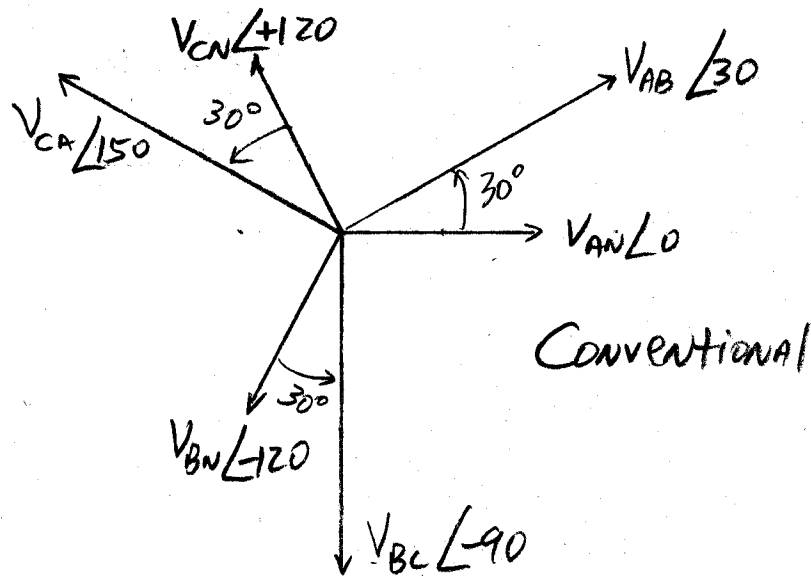


2.6 The phasor diagram with $V_{AN} \angle 0$ is



Since we're given that \tilde{V}_{CA} has angle (-120) instead of angle (150) (Above), all we have to do is work the problem with the conventional angles and then adjust by adding X° , where $X^\circ = (-120 - 150) = -270 = 90^\circ$

$$\tilde{V}_{AN} = \frac{208}{\sqrt{3}} \angle 0 = 120 \angle 0, \quad \tilde{I}_A = \frac{\tilde{V}_{AN}}{Z} = \frac{120 \angle 0}{10 \angle -15^\circ} = 12.0 \angle +15^\circ$$

$$S_{1\phi} = V_{AN} I_A^* = (120 \angle 0)(12.0 \angle -15^\circ) = 1440 \angle -15^\circ \text{ VA} = 1391 \text{ W}$$

$$S_{3\phi} = 3S_{1\phi} = 4320 \angle -15^\circ \text{ VA}$$

$$-j 373 \text{ VAR}$$

Shifting the conventional angles and answers yields

$$\begin{aligned} \tilde{V}_{AN} &= 120 \angle 0 \rightarrow 120 \angle 90^\circ \text{ V} \\ \tilde{V}_{BN} &= 120 \angle 90 - 120 = 120 \angle -30^\circ \text{ V} \\ \tilde{V}_{CN} &= 120 \angle 90 + 120 = 120 \angle 210^\circ \text{ V} = 120 \angle -150^\circ \text{ V} \\ \tilde{V}_{AB} &= 208 \angle 90 + 30 \text{ V} \\ \tilde{V}_{BC} &= 208 \angle -30 + 30 \text{ V} \\ \tilde{V}_{CA} &= 208 \angle -150 + 30 \text{ V} \end{aligned}$$

$$\begin{aligned} \tilde{I}_A &= 12 \angle +15^\circ + 90^\circ = 12 \angle 105^\circ \text{ A} \\ \tilde{I}_B &= 12 \angle 105^\circ - 120 = 12 \angle -15^\circ \text{ A} \\ \tilde{I}_C &= 12 \angle 105^\circ + 120 = 12 \angle 225^\circ \text{ A} \\ &= 12 \angle -135^\circ \text{ A} \end{aligned}$$