

2.7 
$$Y_{TOT} = \frac{1}{Z_C} + \frac{1}{Z_L} + \frac{1}{R} = \frac{1}{-j0.2} + \frac{1}{j0.1} + \frac{1}{10}$$

$$= j5 - j10 + 0.1 = 0.1 - j5 = 5 \angle -88.9^\circ \text{ } \Omega$$

$$I_{TOT} = V Y_{TOT} = (1 \angle 0)(5 \angle -88.9) = 5 \angle -88.9 \text{ A}$$

$$S = V I_{TOT}^* = (1 \angle 0)(5 \angle +88.9) = 5 \angle 88.9$$

$$S = 0.1 + j5, \text{ so } \boxed{P = 0.1 \text{ W}, Q = +5 \text{ VAR}}$$

Easy way - 
$$P = V^2/R = 1^2/10 = \underline{0.1 \text{ W}}$$

$$Q_L = V^2/X_L = 1^2/0.1 = 10 \text{ VAR}$$

$$Q_C = -V^2/X_C = -1^2/0.2 = -5 \text{ VAR}$$

$$Q_{TOT} = (10 - 5) = \underline{5 \text{ VAR}}$$