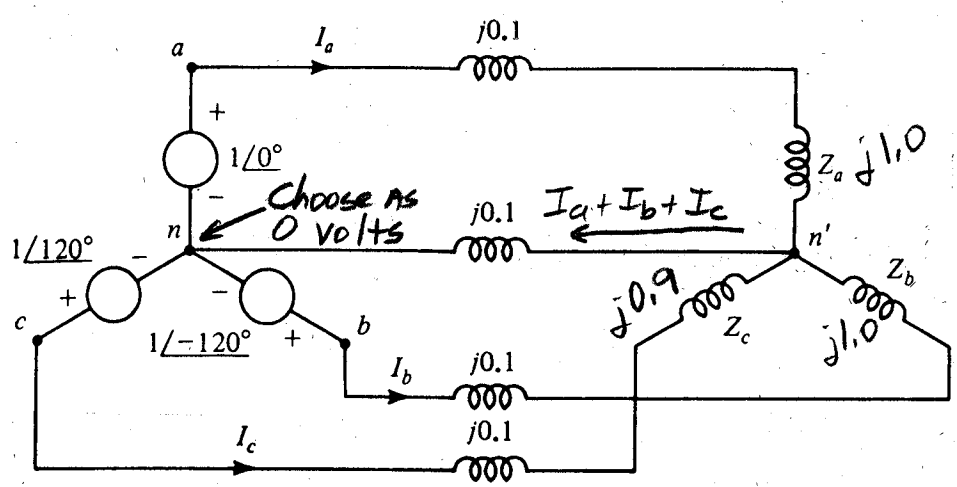


Z.8



a) Unbalanced because $Z_a = Z_b = j1.0$, $Z_c = j0.9$ (but close to balanced). For unbalanced case, we have a conventional circuit problem - can write three mesh current equations, OR one node equation at n' , choosing n as the reference. Obviously, one node equation is easiest!

$$\frac{V_{n'} - V_{an}}{j0.1 + Z_a} + \frac{V_{n'} - V_{bn}}{j0.1} + \frac{V_{n'} - V_{cn}}{j0.1 + Z_b} + \frac{V_{n'} - V_{cn}}{j0.1 + Z_c} = 0$$

Gather terms

$$V_{n'} \left[\frac{1}{j0.1 + j1.0} + \frac{1}{j0.1} + \frac{1}{j0.1 + j1.0} + \frac{1}{j0.1 + j0.9} \right] = \frac{V_{an}}{j0.1 + j1.0} + \frac{V_{bn}}{j0.1 + j1.0} + \frac{V_{cn}}{j0.1 + j0.9}$$

$$V_{n'} [-j0.909 - j1.0 - j0.909 - j1] = \frac{1\angle 0}{j1.1} + \frac{1\angle -120}{j1.1} + \frac{1\angle 120}{j1.0}$$

$$V_{n'} [-j12.8] = -j0.909 \left(1 - \frac{1}{2} - j\frac{\sqrt{3}}{2} \right) - j1 \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right)$$

$$-j12.8 V_{n'} = -j0.455 - 0.787 + j0.5 + 0.866 = 0.079 + j0.045$$

$$V_{n'} = \frac{0.0909\angle 29.7^\circ}{12.8\angle -90^\circ} = 0.0071\angle 119.7^\circ$$

$$\frac{V_{bn}}{j0.1 + j1.0} + \frac{V_{cn}}{j0.1 + j0.9}$$

2.8, cont

$$\text{Now, } \tilde{I}_a = \frac{\tilde{V}_{an} - V_{N'N}}{j0.1 + j1.0} = \frac{1\angle 0 - 0.0071\angle 119.7}{j1.1}$$

And so on. But $V_{N'N}$ is so close to zero that the usual balanced assumption is good.

$$\tilde{I}_a = \frac{\tilde{V}_{an}}{j0.1 + j1.0} = \frac{1\angle 0}{j1.1} = -j0.909\angle 0 = 0.909\angle -90^\circ \text{ A}$$

$$\tilde{I}_b = \tilde{I}_a \angle -120, \quad \tilde{I}_c = \tilde{I}_a \angle 120^\circ$$