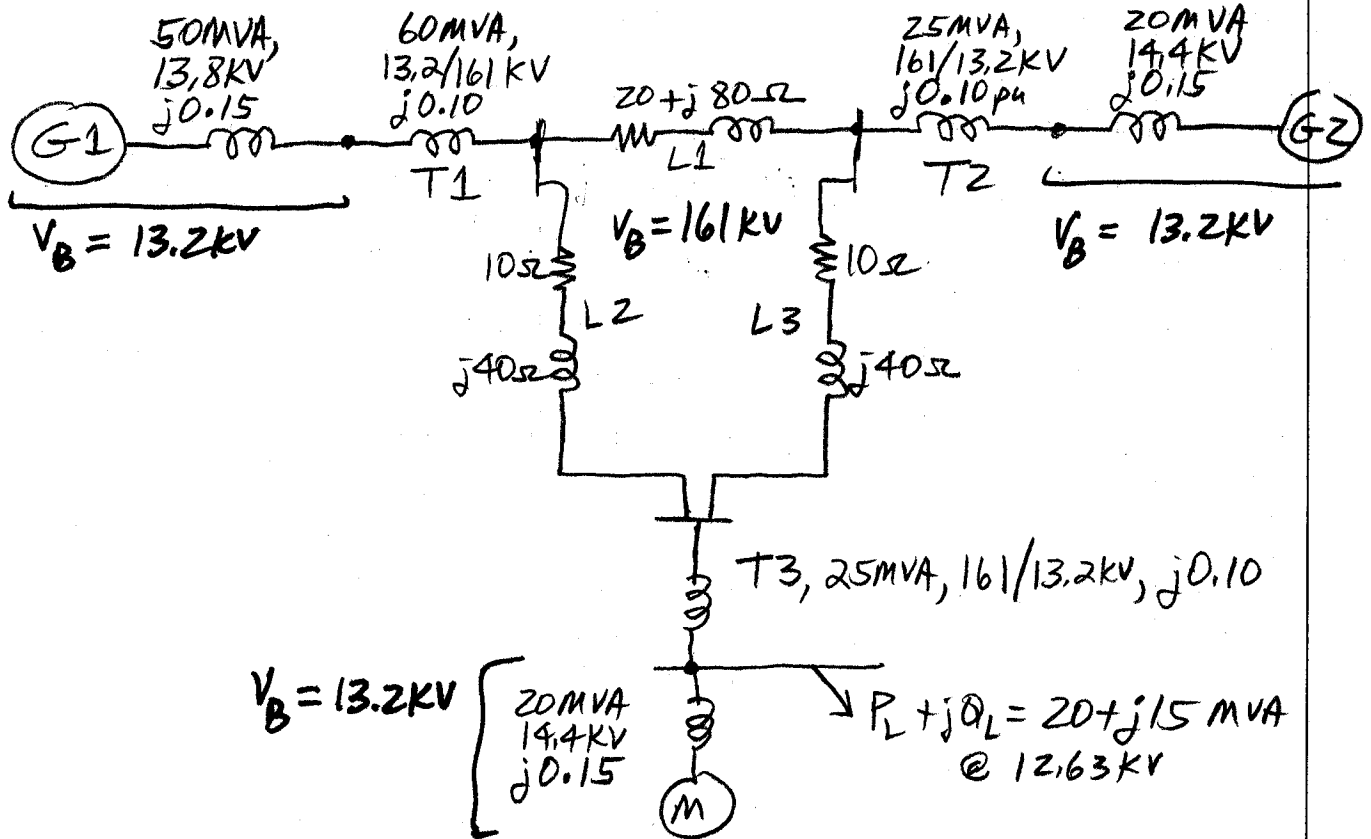


5.19 Use 161 kV base voltage in transmission lines (WASN'T stated in problem), AND 100 MVA



- Setting $V_B = 161$ kV in the transmission lines, the bases AS YOU STEP ACROSS A TRANSFORMER follow the line-to-line turns ratio
- Now, component by component

$$Z_{G1} = j0.15 \left(\frac{100}{50} \right) \left(\frac{13.8}{13.2} \right)^2 = j0.328$$

$$Z_{T1} = j0.10 \left(\frac{100}{60} \right) \left(\frac{13.2}{13.2} \right)^2 = j0.1667$$

FOR transmission lines, $Z_B = \frac{161^2}{100} = 259 \Omega$

$$Z_{L1} = \frac{20 + j80}{259} = 0.0772 + j0.309$$

$$Z_{L2} = Z_{L3} = \frac{10 + j40}{259} = 0.0386 + j0.1544$$


$$Z_{T2} = j0.10 \left(\frac{100}{25} \right) \left(\frac{13.2}{13.2} \right)^2 = j0.40$$

$$Z_{G2} = j0.15 \left(\frac{100}{20} \right) \left(\frac{14.4}{13.2} \right)^2 = j0.893$$

$$Z_{T3} = j0.10 \left(\frac{100}{25} \right) \left(\frac{13.2}{13.2} \right)^2 = j0.40$$

$$Z_M = j0.15 \left(\frac{100}{20} \right) \left(\frac{14.4}{13.2} \right)^2 = j0.893$$

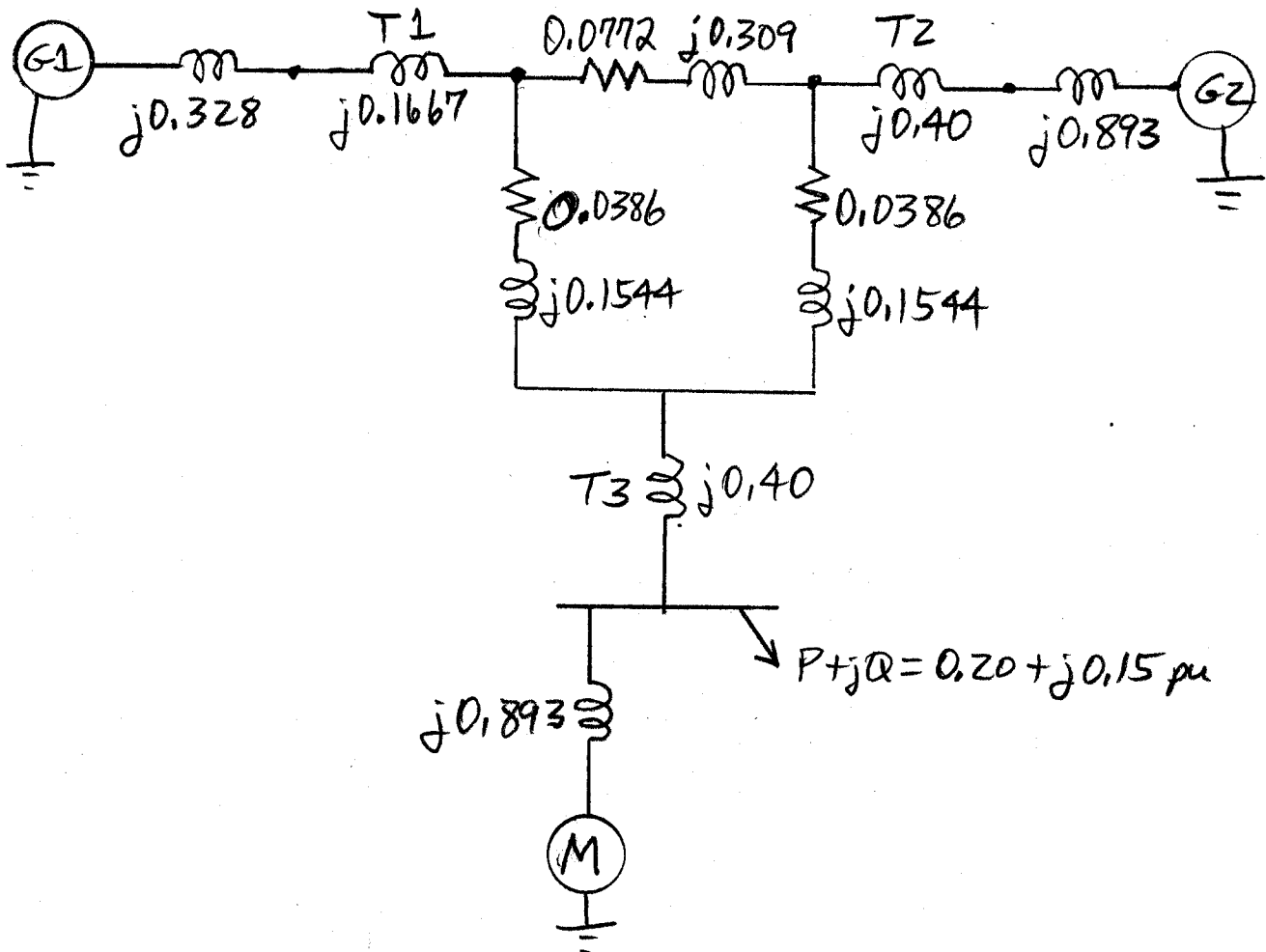For load, we assume constant power, so $P+jQ=0.20+j0.15$



G1, G2, M are represented as voltage sources, Since the network is loaded with $P+jQ$, then we can set the V/S at one gen, but the other gen & motor voltages must be solved by a loadflow program where gen & motor P, Q are known