
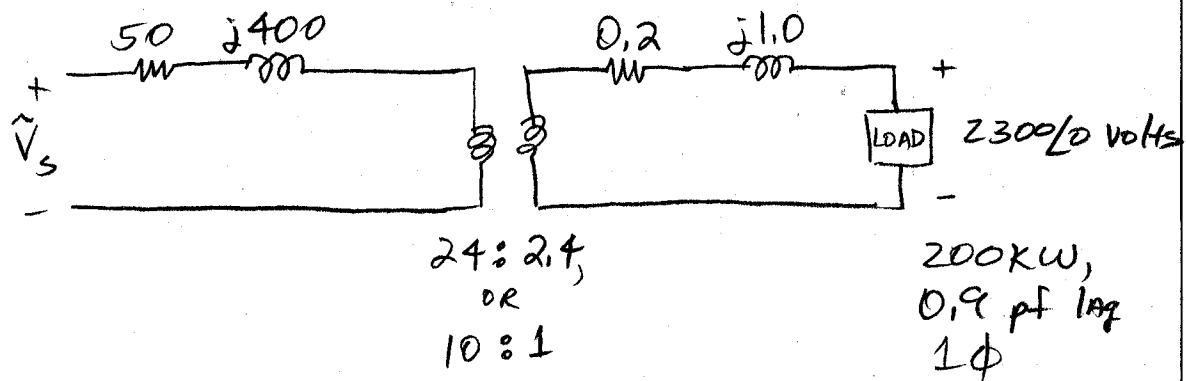


5.5

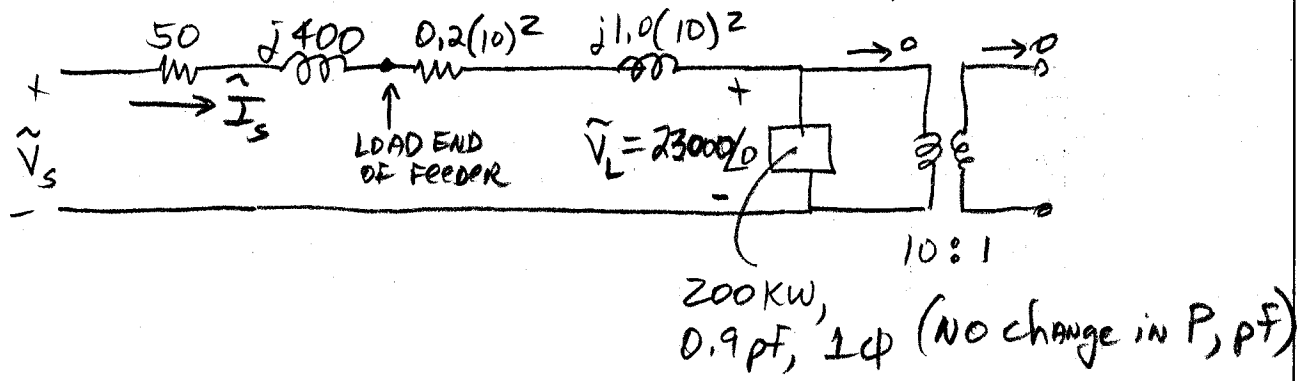

Reflect all to the 24kV side makes the problem easier



You can also think of the load connection as a shorted transformer in series with the load

Get \tilde{I}_s from the load condition,

$$\tilde{V}_L \tilde{I}_s^* = S_L = \frac{P_L}{\text{pf}} \angle \cos^{-1}(\text{pf}) = \frac{200000}{0.9} \angle +25.8^\circ$$

↑ lagging current gives +Q

$$\tilde{I}_s^* = \frac{222000 \angle 25.8^\circ}{23000 \angle 0} = 9.65 \angle 25.8$$

$$\tilde{I}_s = 9.65 \angle -25.8 \text{ A}$$

$$\tilde{V}_s = \tilde{V}_L + \tilde{I}_s z = (23000 \angle 0) + (9.65 \angle -25.8)(50 + j400 + 20 + j100)$$

$$= 23000 + (9.65 \angle -25.8)(505 \angle 82^\circ)$$

$$\tilde{V}_s = 23000 + 4873 \angle 56.2 = 23000 + 2711 + j4049$$

ⓐ $\tilde{V}_s = 25711 + j4049 = 26028 \angle 8.9^\circ \text{ V}$ (a 13% rise in mag) from the load

5,5, cont

At the load end of the feeder,

$$\begin{aligned}\tilde{V}_{\text{Feed}} &= 23000 \angle 0 + (9.65 \angle -25.8)(20 + j100) \\ &= 23000 \angle 0 + 984 \angle 52.9 \quad 102.0 \angle 78.7\end{aligned}$$

$$\textcircled{b} \quad \tilde{V}_{\text{Feed}} = 23000 + 594 + j784 = 23594 + j784 = 23607 \angle 1.9^\circ$$

a 2.6% rise

$$\textcircled{c} \quad S_s = \tilde{V}_s \tilde{I}_s^* = (26028 \angle 8.9)(9.65 \angle -25.8) = 251170 \angle -34.7$$

$$S_s = 206498 + j142986$$

$P_s + jQ_s$

$$P_L = 200000$$

$$\eta = \frac{P_L}{P_s} = \frac{200000}{206498} = 0.969$$

$$\text{Also, } \eta = \frac{P_L}{P_L + P_{\text{loss}}} = \frac{200000}{200000 + (9.65)^2(50 + 20)} = 0.968$$

ckt resistance

$$\text{If no load, } |\tilde{V}_L| = |\tilde{V}_s| = 26028$$

$$\begin{aligned}\text{so } \% V_{\text{reg}} &= \frac{|V_L|_{\text{NL}} - |V_L|_{\text{FL}}}{|V_L|_{\text{FL}}} = \frac{26028 - 23000}{23000} \cdot 100\% \\ &= \underline{\underline{13.2\%}}\end{aligned}$$