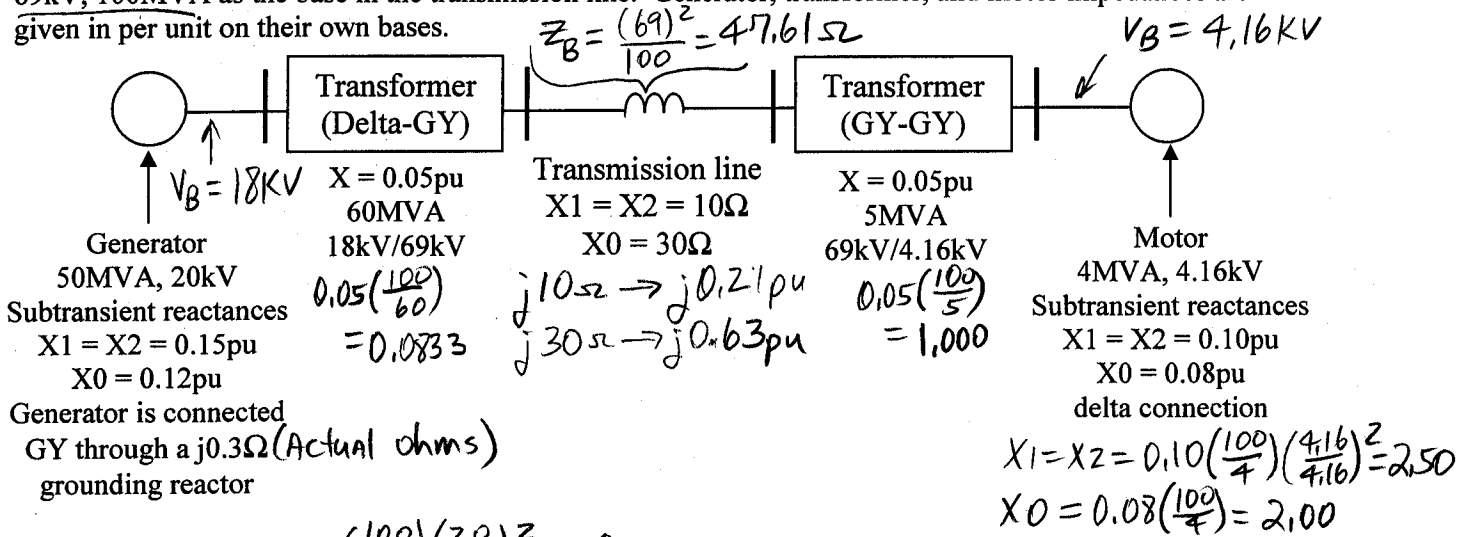


Six equally-weighted problems. Three sheets of notes permitted. Show all work.

Problem 1. Draw the positive, negative, and zero-sequence one-line diagrams for the system shown. Use 69kV, 100MVA as the base in the transmission line. Generator, transformer, and motor impedances are given in per unit on their own bases.




For gen, $X_1 = X_2 = 0.15 \left(\frac{100}{50}\right) \left(\frac{20}{18}\right)^2 = 0.370 \text{ pu}$


$X_0 = 0.12 \left(\frac{100}{50}\right) \left(\frac{20}{18}\right)^2 = 0.296 \text{ pu}$

REACTOR, $Z_B = \frac{(18)^2}{100} = 3.24$, so $j0.3 \Omega$ becomes $j0.0926 \text{ pu}$

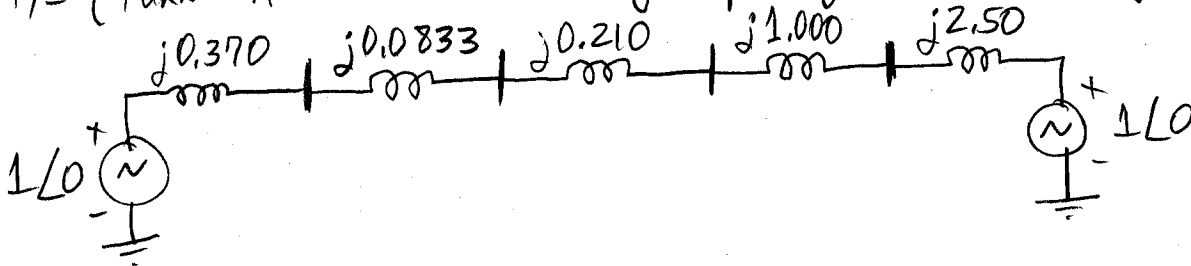
+/- (Turn off sources for - by replacing the 1LO voltage with a short)



0 seq.

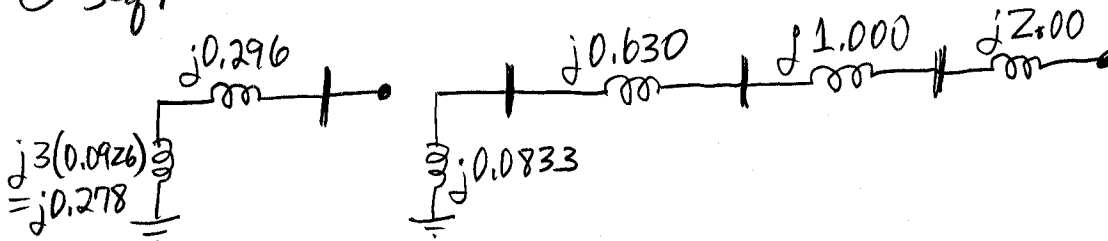

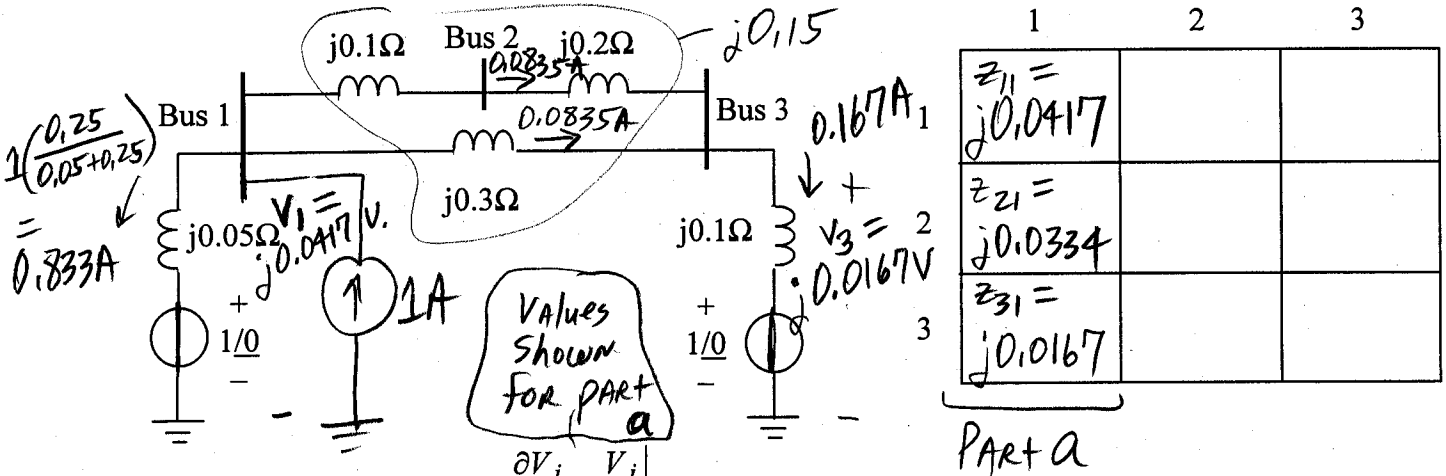Problem 2. The positive-sequence one-line diagram for a network is shown below. The ground ties at busses 1 and 4 represent the subtransient impedances of machines. Prefault voltages are all 1.0pu.



a. Use the definition $z_{jk} = \frac{\partial V_j}{\partial I_k} = \frac{V_j}{I_k} \Big|_{I_m=0, m \neq k}$ to fill in column 1 of the Z matrix.

Now, a solidly-grounded three-phase fault occurs at bus 1. z_{11} Check, $j0.05 \parallel (j0.15 + j0.10) = j0.0417$ (OK)

b. Compute the fault current

c. Use the fault current and Z matrix terms to compute the voltages at busses 2 and 3.

d. Find the magnitude of the current flowing in the line connecting busses 2 and 3.

$$b. I_{1a}^F = \frac{V_{1a}^{pre}}{z_{11}} = \frac{1}{j0.0417}$$

$$I_{1a}^F = -j24.0A$$



$$V_2 = V_3 + j0.2 \left(\frac{0.167}{2} \right) = j0.0334$$

$$c. V_{2a}^F = V_{2a}^{pre} - z_{21} I_{1a}^F = 1.0 - (j0.0334)(-j24) = 1.0 - 0.800 = 0.200V$$

$$V_{3a}^F = V_{3a}^{pre} - z_{31} I_{1a}^F = 1.0 - (j0.0167)(-j24) = 1.0 - 0.401 = 0.600V$$

$$d. I_{23}^F = \frac{V_2^F - V_3^F}{j0.2} = \frac{0.2 - 0.6}{j0.2} = j2.0$$

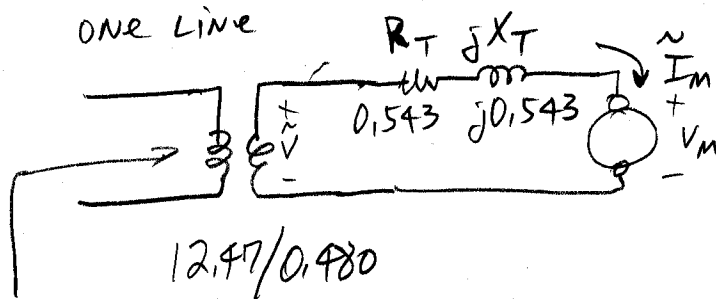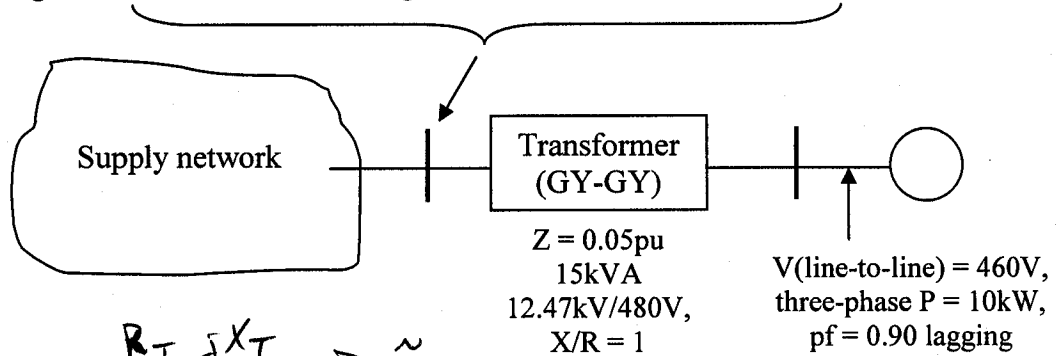Problem 3. Find the magnitude of the line-to-line voltages on the 12.47kV side of the transformer.



Want line-to-line voltage here

$$V_m I_m^* = S_m \angle \phi, \quad I_m = \frac{S_m \angle \phi}{V_m^*}$$

$$I_m = \frac{\frac{10000}{3(0.9)} \angle \cos^{-1}(0.9)}{\frac{460}{\sqrt{3}} \angle 0} = 13.95 \angle -25.8^\circ \text{ A}$$

$R_T + jX_T$ is TRANSFORMER impedance on 480V side

$$Z_B = \frac{(480)^2}{15000} = 15.36 \Omega$$

$$Z_T = (0.05)(15.36) = 0.768 \Omega$$

$$\frac{Z_T}{R_T} \angle 45^\circ = \frac{X_T}{R_T} = 1, \quad \text{so } 45^\circ, \text{ so } R_T = X_T = \frac{Z_T}{\sqrt{2}}$$

$$R_T = X_T = 0.543$$

$$\tilde{V} = \tilde{V}_m + \tilde{I}_m Z_T = \frac{460}{\sqrt{3}} \angle 0 + (13.95 \angle -25.8^\circ)(0.768 \angle 45^\circ)$$

$$= 266 + 10.71 \angle -19.2^\circ = 266 + 10.11 - j3.52 = 276 - j3.52$$

$\tilde{V} = 276 \angle -0.73^\circ$, so on the 12.47kV side,


$$|\tilde{V}_{LL}| = (\sqrt{3})(276) \left(\frac{12.47}{0.480} \right) = \boxed{12419 \text{ V}}$$

Six equally-weighted problems. Three sheets of notes permitted. Show all work.

Problem 4. Consider the 69kV, ^{60Hz} transmission line shown below. The phases have single conductors.

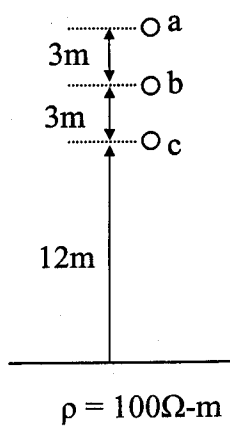- a. Find the positive sequence R, L, and C per meter for the transmission line shown.
- b. Convert the above values to series (R + jX), and shunt MVAR, per km, using a base of 69kV, 100MVA.

Conductors have outer radius 1cm, and resistance 0.06 Ω per km



For CAP, $r = 1\text{cm}$. For ind, $r_{\text{eff}} = r e^{-1/4} = 0.7788\text{cm}$

$$GMD_{+-} = (3 \cdot 6 \cdot 3 \cdot 3 \cdot 3 \cdot 6)^{1/6} = 3.78\text{m}$$

$$C_{+-} = \frac{2\pi\epsilon_0}{\ln \frac{GMD_{+-}}{r}} = \frac{2\pi(8.854)}{\ln \frac{3.78}{0.01}} \text{ pF/m} = 9.37 \text{ pF/m}$$

$$L_{+-} = \frac{\mu_0}{2\pi} \ln \frac{GMD_{+-}}{r_{\text{eff}}} = \frac{4\pi \times 10^{-7}}{2\pi} \ln \frac{3.78}{0.007788} = 1.237 \text{ } \mu\text{H/m}$$

$$R_{+-} = 0.06 \text{ } \Omega/\text{km}$$

So, $R_{+-} = 6 \times 10^{-5} \text{ } \Omega/\text{m}$
 (a) $C_{+-} = 9.37 \text{ pF/m}$
 $L_{+-} = 1.237 \text{ } \mu\text{H/m}$


(b) $Z_B = \frac{(69)^2}{100} = 47.61 \text{ } \Omega$. $R = \frac{0.06 \text{ } \Omega/\text{km}}{47.61} = 0.001260 \text{ pu/km}$

$j\omega L = j(120\pi)(1.237 \times 10^{-6})(1000) = j0.466 \text{ } \Omega/\text{km} = j0.00980 \text{ pu/km}$

$Q_{\text{cap}} = 3 V_{LN}^2 \omega C = (3) \left(\frac{69000}{\sqrt{3}}\right)^2 (120\pi)(9.37 \times 10^{-12})(1000) = 16.82 \text{ KVAR/km}$

$Q_{\text{cap ph}} = \frac{16.82 \times 10^3}{100 \times 10^6} = 0.000168 \text{ VAR/km}$

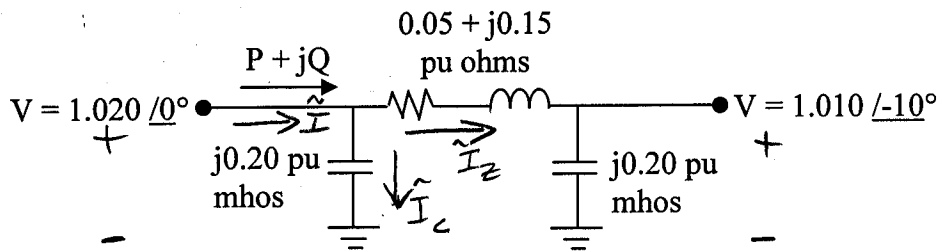Problem 5. Calculate the P and Q flows (in per unit) for the loadflow situation shown below.



$$P + jQ = V \tilde{I}^* = V (\tilde{I}_c + \tilde{I}_2)^*$$

$$\hat{I}_2 = \frac{1.020 \angle 0^\circ - 1.010 \angle -10^\circ}{0.05 + j0.15} = \frac{1.02 - (0.995 - j0.1754)}{0.1581 \angle 71.6^\circ}$$

$$\hat{I}_2 = \frac{0.0250 + j0.1754}{0.1581 \angle 71.6^\circ} = \frac{0.11772 \angle 81.9^\circ}{0.1581 \angle 71.6^\circ} = 1.121 \angle 10.3^\circ$$

$$\tilde{I}_2 = 1.103 + j0.200$$

$$\hat{I}_c = \tilde{V} Y_c = (1.02 \angle 0^\circ)(0.20 \angle 90^\circ) = 0.204 \angle 90^\circ = j0.204$$

$$\tilde{I} = \hat{I}_2 + \hat{I}_c = 1.103 + j0.404 = 1.175 \angle 20.1^\circ$$

$$P + jQ = (1.020 \angle 0^\circ)(1.175 \angle 20.1^\circ)^* = 1.199 \angle -20.1^\circ$$


$$P + jQ = \frac{1.126}{P} - j \frac{0.412}{Q} \quad Q = -0.412$$

Six equally-weighted problems. Three sheets of notes permitted. Show all work.

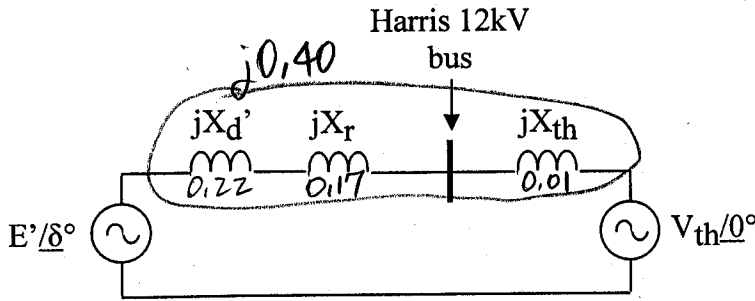Problem 6. A new 32MVA, 60Hz steam generator was recently installed at the UT power plant. The generator is connected through a large reactor to ERCOT at the Harris 12kV bus.

The electrical diagram and internal voltage (for the transient condition) that exists when the generator is producing (25MW + j12.4MVar) is shown below. Suddenly, at $t = 0$, a three-phase fault with zero impedance occurs at the Harris 12kV bus. ~~The fault is successfully removed in 6 cycles (of 60Hz).~~

Assuming that E' , V_{th} , and P_{mech} are constant, ~~use the equal area criterion to find the maximum value that δ achieves.~~ Use the attached graph to show important P and δ points and lines on the power curve, and show clearly which areas are being set equal. *determine the critical clearing time (in cycles).*



- Machine $E' = 1.100$ pu
- Machine $\delta = 16.5^\circ$
- Machine $P = 25$ MW (i.e., 0.781 pu)
- Machine $jX_{d'} = j0.22$ pu
- Machine $H = 1.4$ seconds
- Reactor $jX_r = j0.17$ pu
- Thevenin $jX_{th} = j0.01$ pu
- Thevenin $V_{th} = (1.0 + j0)$ pu
- Values given on the generator base

Remember that during the fault, the electrical power output is zero, and thus the rotor accelerates

according to $\delta(t) = \frac{\omega_s P_{mech}}{4H} t^2 + \delta(t=0)$. Also, note that $\omega_s = 377$ rad/sec, δ is in radians in the

above formula, and P_{mech} is in pu. $S_{crit} = \cos^{-1} \left[\frac{(\pi - 2S_0) \sin(S_0) - \cos(S_0)}{0.729} \right]$

$S_0 = 16.5^\circ$, so $S_{crit} = \cos^{-1} \left[\frac{(\pi - 2(0.288)) \sin(16.5^\circ) - \cos(16.5^\circ)}{0.729} \right]$
 $= 0.288$ rad

$S_{crit} = 103.3^\circ$
 $= 1.803$ rad

Use $S(t) = \frac{\omega_s P_{mech}}{4H} t^2 + S_0$ to get $t^2 = \frac{4H}{\omega_s P_{mech}} (S_{crit} - S_0)$


$t^2 = \frac{4(1.4)}{(377)(0.781)} (1.803 - 0.288)$

$t = 0.1697$ sec = 10.18 cycles of 60 Hz

On curve,

$P_{max} = \frac{E' V_{th}}{j0.40} \sin 90^\circ = 2.75$

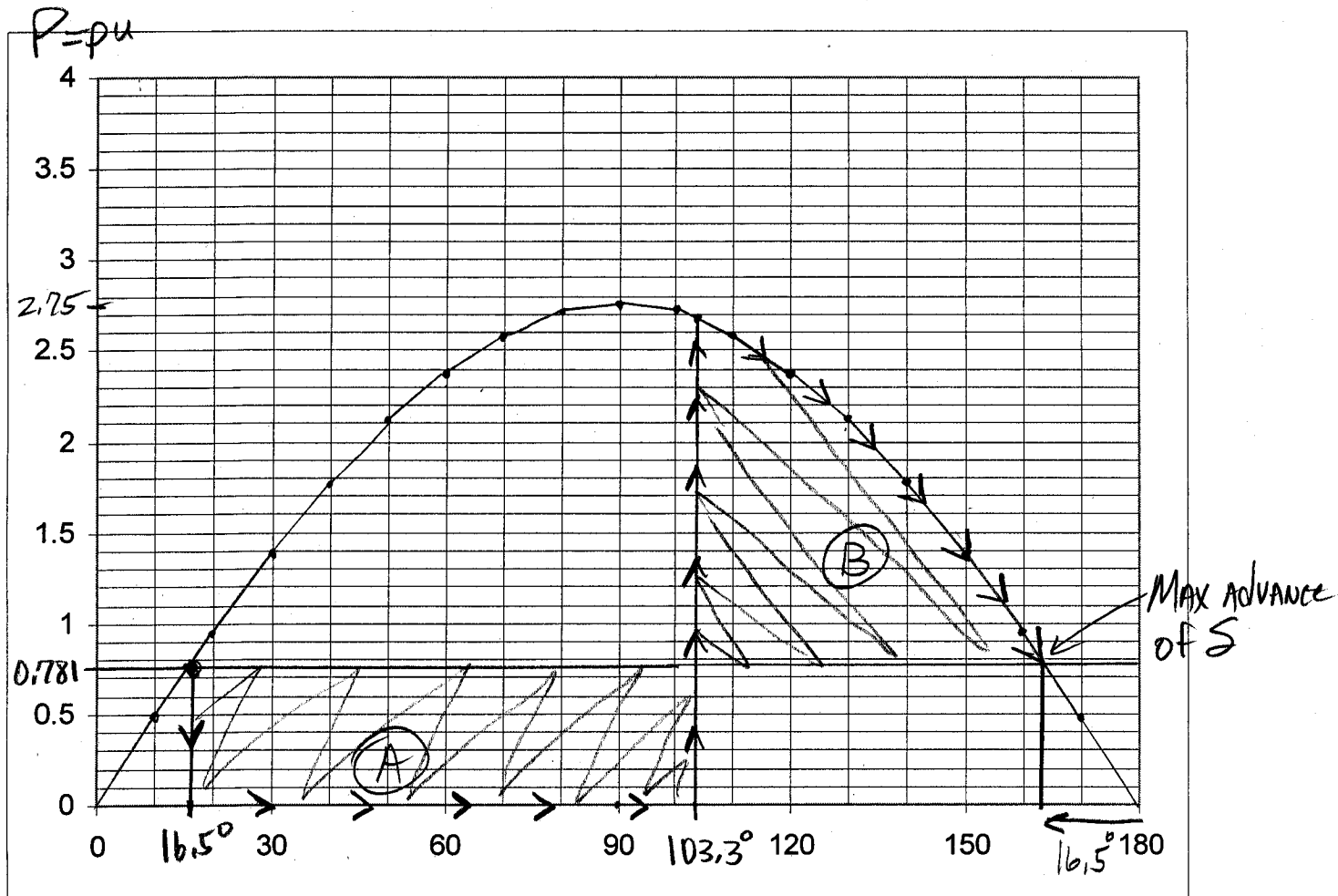Six equally-weighted problems. Three sheets of notes permitted. Show all work.



→
S movement

AREAS (A) = (B)
 ↑ S Accelerating
 ← S decelerating