

6.2


$$V_a I_a^* = S_g, \quad I_a^* = \frac{S_g}{V_a} = \frac{1 \angle 45}{1 \angle 0} = 1 \angle 45, \quad I_a = 1 \angle -45$$

$$\begin{aligned} \text{Find } a' &= V_a + V_a I_a + j X_g I_a \text{ to locate the } g\text{-axis} \\ &= 1 \angle 0 + (0) I_a + j 0.9 (1 \angle -45) = 1 \angle 0 + 0.9 \angle 45 \\ &= (1 + j0) + (0.636 + j0.636) = 1.636 + j0.636 \end{aligned}$$

$$a' = 1.755 \angle 21.2^\circ \text{ V}$$

So, since V_a has ref. angle 0° , $\delta = 21.2^\circ$

$$\text{Find } I_{ad}, I_{ag}. \quad I_{ad} = |I_a| \sin(\delta - \angle I_a) = 0.915 \text{ pu} = I_{ad}$$

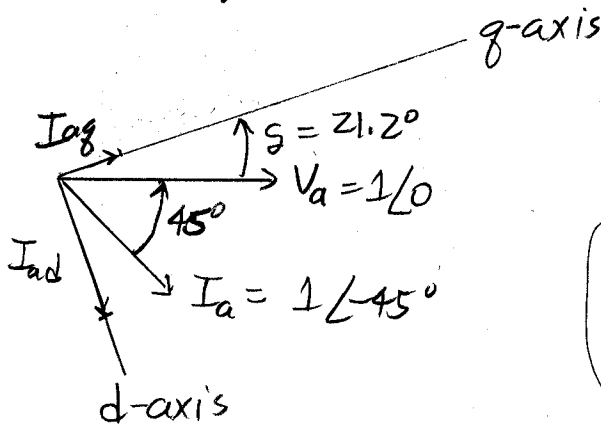

$$\begin{aligned} I_{ag} &= |I_a| \cos(\delta - \angle I_a) \\ &= 0.404 \text{ pu} \end{aligned}$$

$$\begin{aligned} \text{So, } I_{ad} &= 0.915 \angle \delta - 90^\circ \\ &= 0.915 \angle +68.8^\circ \end{aligned}$$

$$I_{ag} = 0.404 \angle \delta = 21.2^\circ$$

$$\begin{aligned} \text{Find } E_a &= V_a + r I_a + j X_d I_{ad} + j X_g I_{ag} \\ &= 1 + j 1.6 (0.915 \angle 68.8) + j 0.9 (0.404 \angle 21.2) \\ &= 1 + 1.464 \angle 21.2 + 0.364 \angle 111.2 \\ &= 1 + 1.365 + j 0.529 = 2.365 + j 0.529 \\ &= 2.43 + j 0.868 \end{aligned}$$

$$E_a = 2.39 \angle 21.2 \text{ pu} \quad (\text{Angle checks with } \delta)$$

overexcited
because $\angle I_a$ is lagging, so E_a is large

$$6.4 \quad S_g = V_a I_a^* = (1 \angle 0)(1 \angle +60)^* = 1 \angle -60$$

$$a' = V_a + V_a I_a + j X_g I_a = 1 + (0.1)(1 \angle 60) + j(0.6)(1 \angle 60)$$

$$a' = 1 + 0.1 \angle 60 + 0.6 \angle 150 = 1 + 0.05 + j0.0866 - 0.520 + j0.3$$

$$a' = 0.53 + j0.387 = 0.656 \angle 36.1^\circ$$

So, the q -axis is at 36.1°

$$|I_{aq}| = |I_a| \cos(\delta - \angle I_a) = 1 \cos(36.1 - 60) = 1 \cos(-23.9)$$

$$I_{aq} = 0.914 \angle -5 = 0.914 \angle 36.1$$

$$|I_{ad}| = |I_a| \sin(\delta - \angle I_a) = 1 \sin(36.1 - 60) = -0.405$$

$$I_{ad} = -0.405 \angle 36.1 - 90^\circ = -0.405 \angle -53.9 = 0.405 \angle 126.1$$

$$I_{ad} = 0.405 \angle 126.1$$

$$\tilde{E}_a = V_a + V_a I_a + j X_d I_{ad} + j X_g I_{aq}$$

$$= 1 + (0.1)(1 \angle 60) + j(1.0)(0.405 \angle 126.1) + j(0.6)(0.914 \angle 36.1)$$

$$= 1 + 0.1 \angle 60 + 0.405 \angle 216.1 + 0.548 \angle 126.1$$

$$= 1 + 0.05 + j0.0866 - 0.327 - j0.239 - 0.323 + j0.443$$

$$= 0.400 + j0.291$$

$$= 0.495 \angle 36.1 \quad \leftarrow \text{Underexcited because}$$


checks with S

$\angle I_a$ is leading so


E_a is small

Steady State Model for Round Rotor Machine

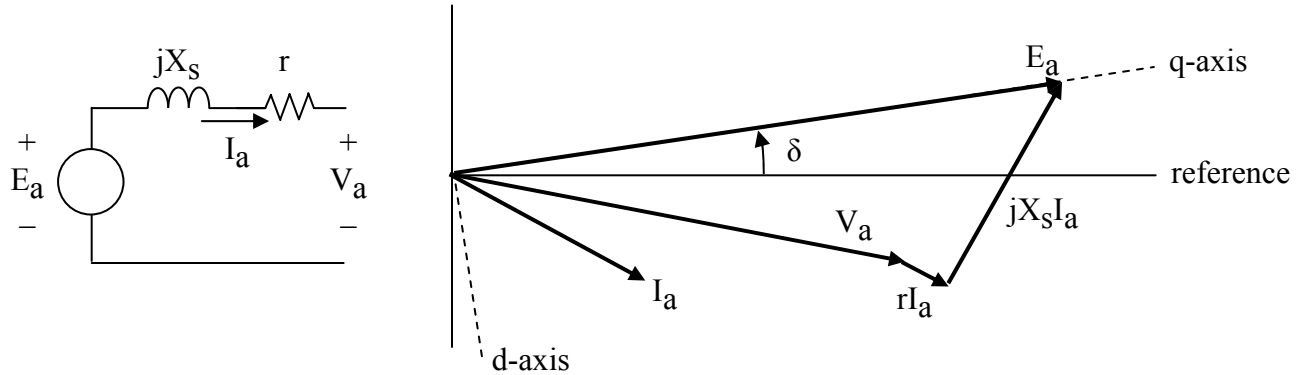V_a and I_a are the terminal voltage and current. X_s is the synchronous reactance. Resistance r is the stator resistance. E_a is the Thevenin equivalent voltage behind synchronous reactance.



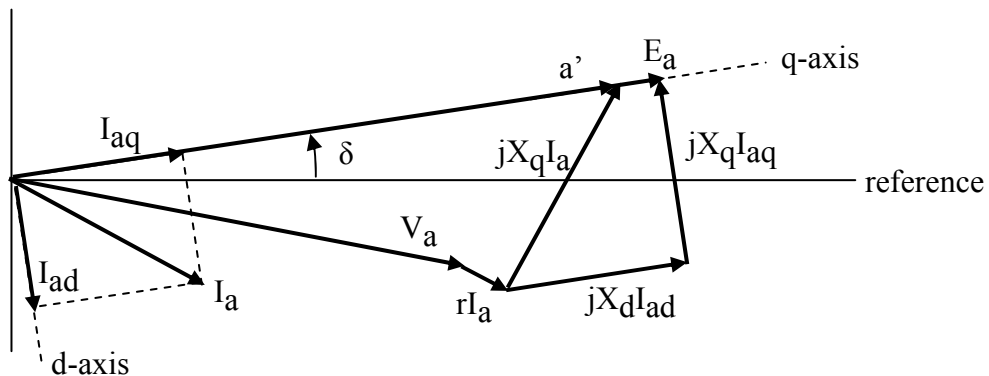Steady-State Model for Salient Pole Machine (No equivalent circuit. Phasor diagram only)




Steps when V_a and I_a are known:


- With V_a , I_a , r , and X_q , find phasor a' to locate the q-axis.
- Then, compute I_a projections I_{aq} and I_{ad} where
 - I_{aq} has magnitude $|I_a| \cos(\delta - \angle I_a)$ and has phase angle δ ,
 - I_{ad} has magnitude $|I_a| \sin(\delta - \angle I_a)$ and has phase angle $(\delta - 90^\circ)$,
 and where $\angle I_a$ is the angle of I_a .
- Then, find E_a .

Transient Stability Machine Model 1 Constant Voltage Magnitude E' Behind Transient Reactance X_d'

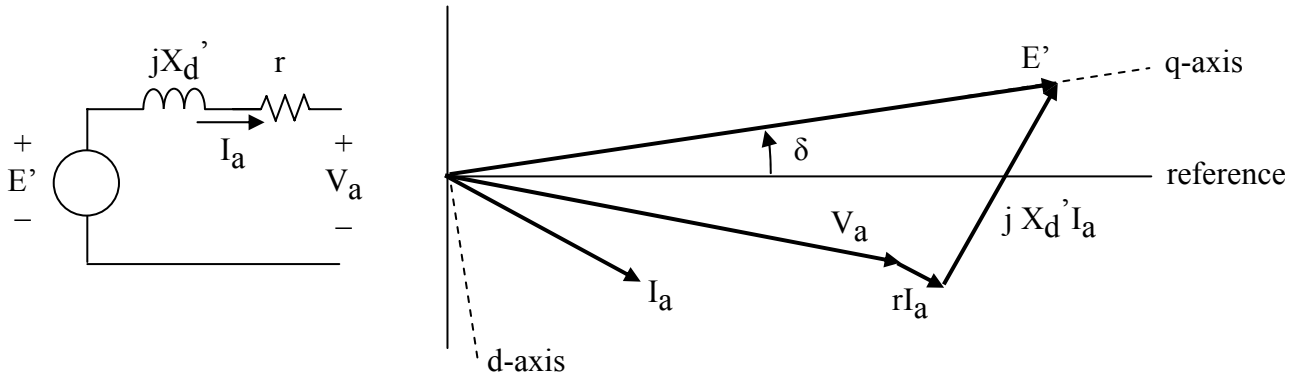This model is like the round rotor synchronous model, except that the transient reactance is used instead of the synchronous reactance.



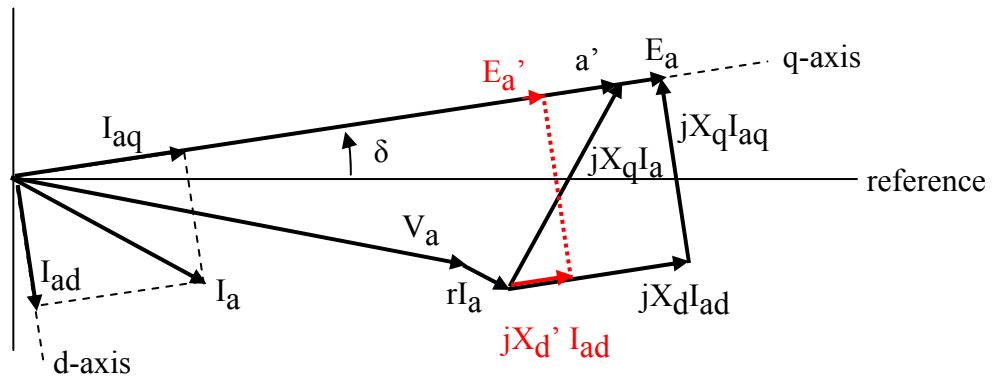Transient Stability Machine Model 2 Salient Pole Rotor



Steps when V_a and I_a are known: Begin with same steps used in the salient pole synchronous machine model. Then, use X_d' and I_{ad} to find $E_{a'}$.

The magnitude of $E_{a'}$ varies according to $\frac{d|E_{a'}|}{dt} = \frac{1}{T'_{do}}(E_{fd} - |E_a|)$, where T'_{do} is the direct-axis transient open circuit time constant, and E_{fd} is the field voltage (as seen from the stator). As a first approximation, E_{fd} is treated as a constant whose initial value is the same as the initial value of $|E_a|$.