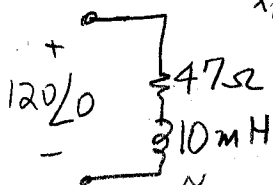


Problem 1. A load consists of a 47Ω resistor and 10mH inductor in series. The load is energized by a 120V, 60Hz voltage source. The phase angle of the voltage source is zero.

- Determine the phasor current
- Determine the load P, pf, Q, and S.
- Find an expression for instantaneous p(t)



$$X_L = 2\pi fL = (2\pi)(60)(10 \times 10^{-3}) = 1200\pi \times 10^{-3} = 3.77 \Omega$$

$$Z_L = 47 + j3.77 \Omega = 47.2 / 4.59^\circ$$

$$a) \tilde{I} = \frac{\tilde{V}}{Z_L} = \frac{120 \angle 0}{47.2 / 4.59}$$

$$\tilde{I} = 2.54 \angle -4.59 \text{ A (RMS)}$$

$$b) S = VI^* = (120 \angle 0)(2.54 \angle -4.59) = 305 \angle -4.59 \text{ VA}$$

$$P = \text{Re}\{S\} = 305 \cos(4.59^\circ) = 304 \text{ W}$$

$$Q = \text{Im}\{S\} = 305 \sin(4.59^\circ) = 24.4 \text{ VAR}$$

$$\text{pf} = \cos(4.59^\circ) = 0.997$$

$$\text{Also, } P = |I|^2 R = (2.54)^2 (47) = 303 \text{ W}$$

$$Q = |I|^2 X_L = (2.54)^2 (3.77) = 24.3 \text{ VAR}$$

$$\frac{|S| = 305}{P = 304} Q = 24.4$$


$$c) p(t) = V_p \cos(\omega t + \theta_V) I_p \cos(\omega t + \theta_I) = \frac{V_p I_p}{2} [\cos(\theta_V - \theta_I) + \cos(2\omega t + \theta_V + \theta_I)]$$

$$p(t) = 305 [0.997 + \cos(754t - 4.59^\circ)] \quad (\text{Note, } P = 305(0.997) = 304 \text{ W})$$

Problem 2. A three-phase, 460V motor draws 5kW with a power factor of 0.80 lagging. Assuming that \tilde{V}_{an} has phase angle zero,

- Find phasor currents \tilde{I}_a and \tilde{I}_{ab} (note - \tilde{I}_{ab} is inside the motor delta windings)
- Find the three phase motor Q and S
- How much capacitive kVAR (three-phase) should be connected in parallel with the motor to improve the net power factor to 0.95?

a) DRAW A ONE-LINE DIAGRAM

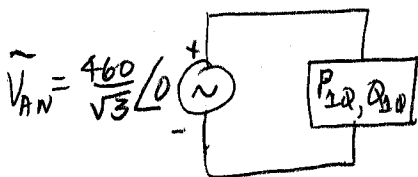

$$P_{1\phi} = \frac{P_{3\phi}}{3} = \frac{5000}{3} = 1667 \text{ W}$$

$$Q_{1\phi} = P_{1\phi} \sqrt{\left(\frac{1}{\text{PF}}\right)^2 - 1} = 1250 \text{ VAR}$$

$$S_{1\phi} = \frac{P_{1\phi}}{\text{PF}} \angle \cos^{-1}(\text{PF}) = \frac{1667}{0.80} \angle 36.9^\circ = 2084 \angle 36.9 \text{ VA}$$

$$\frac{S_{1\phi} = 2084}{P_{1\phi} = 1667} Q_{1\phi} = 1250 \text{ VAR}$$

$$a) S_{1\phi} = V_{AN} (I_A)^* \Rightarrow I_A = \frac{S_{1\phi}^*}{V_{AN}^*} = \frac{2084 \angle -36.9}{\frac{460}{\sqrt{3}} \angle 0} = 7.85 \angle -36.9 \text{ A}$$

$$\tilde{I}_{ab} = \frac{\tilde{I}_a}{\sqrt{3}} \angle 30^\circ = \frac{7.85 \angle -36.9}{\sqrt{3}} \angle 30 = 4.53 \angle -6.9^\circ \text{ A} = \tilde{I}_{ab}$$

$$b) Q_{3\phi} = 3 Q_{1\phi} = 3750 \text{ VAR}$$

$$Q_{3\phi} = P_{3\phi} \sqrt{\left(\frac{1}{\text{PF}}\right)^2 - 1} = 3750$$

$$S_{3\phi} = 3 S_{1\phi} = 6252 \angle 36.9 \text{ VA}$$

$$c) Q_{\text{NET}} = P_{\text{NET}} \sqrt{\left(\frac{1}{\text{PF}_{\text{NET}}}\right)^2 - 1} = 5000 \sqrt{\left(\frac{1}{0.95}\right)^2 - 1} = 1643 \text{ VAR}$$

$$Q_{\text{NET}} = Q_{\text{MOT}} + Q_{\text{CAP}}, Q_{\text{CAP}} = 1643 - 3750 = -2107 \text{ VAR}$$