
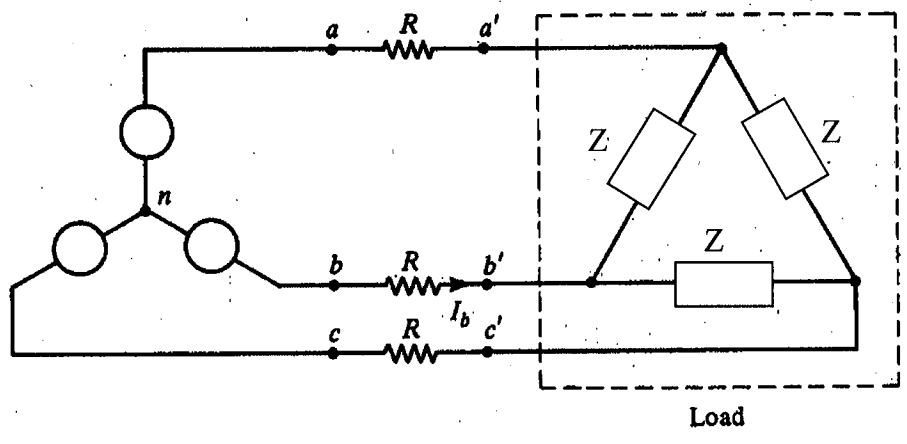


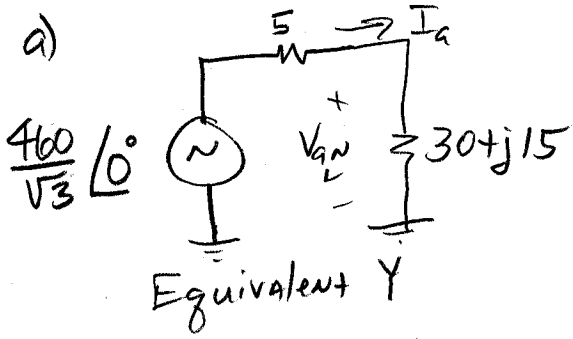The 60Hz system shown below is balanced. The line-to-line voltage of the source is 460V. Resistors R are each 5Ω.



Part a. If each Z is $(90 + j45)\Omega$, determine the three-phase complex power delivered by the source, and the three-phase complex power absorbed by the delta-connected Z loads.

Part b. If \tilde{V}_{an} at the source has phase angle zero, find $\tilde{V}_{a'b'}$ at the load.



$$\tilde{I}_a = \frac{460 \angle 0}{\sqrt{3} \cdot 35 + j15} = \frac{266 \angle 0}{38.1 \angle 23.2^\circ} = 6.98 \angle -23.2^\circ$$

$$P_{L1\phi} = |I_a|^2 R_{LY} = (6.98)^2 (30) = 1462 \text{ W}$$

$$Q_{L1\phi} = |I_a|^2 X_{LY} = 731 \text{ VAR}$$

$$S_{L1\phi} = P_{L1\phi} + jQ_{L1\phi} = 1635 \angle 26.6^\circ \text{ VA}$$

Source

$$3 \tilde{V}_{an} \tilde{I}_a^*$$

$$= 3 \left(\frac{460}{\sqrt{3}} \angle 0 \right) (6.98 \angle 23.2)$$

$$= 5561 \angle 23.2 \text{ VA}$$

$$5111 + j2191$$

$$S_{L3\phi} = 3 S_{L1\phi} = 4905 \angle 26.6 \text{ VA}$$

$$4385 + j2196$$

b)


$$\tilde{V}_{an} = \tilde{I}_a Z_Y = (6.98 \angle -23.2^\circ) (30 + j15) = 234 \angle 3.4^\circ$$

$$33.5 \angle 26.6$$

$$\tilde{V}_{ab} = \sqrt{3} \tilde{V}_{an} \cdot 1/30$$

$$\tilde{V}_{ab} = (\sqrt{3}) (234 \angle 3.4^\circ) (1/30) = 405 \angle 33.4^\circ \text{ V}$$

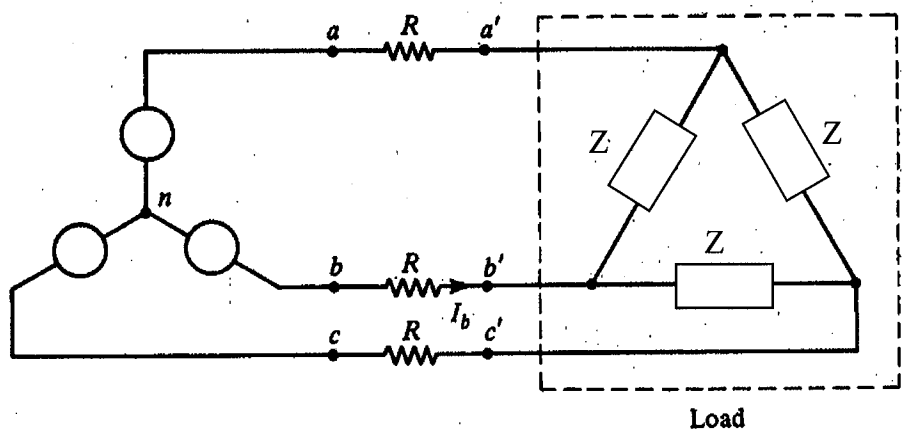
The 60Hz system shown below is balanced. The line-to-line voltage of the source is 460V. Resistors R are each 4Ω.



Part a. If each Z is $(80 + j40)\Omega$, determine the three-phase complex power delivered by the source, and the three-phase complex power absorbed by the delta-connected Z loads.

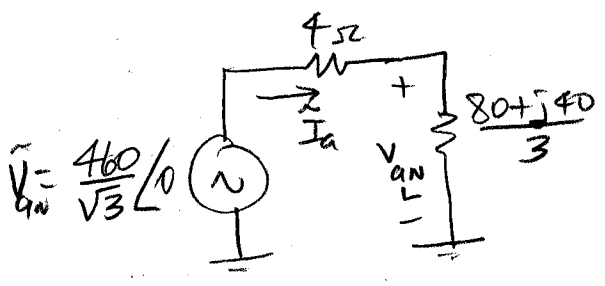Part b. If \tilde{V}_{an} at the source has phase angle zero, find $\tilde{V}_{a'b'}$ at the load.

Convert the load to a Y, where $Z_Y = \frac{80 + j40}{3}$



$$\tilde{I}_a = \frac{\tilde{V}_{an}}{4 + \frac{80 + j40}{3}} = \frac{\frac{460}{\sqrt{3}} \angle 0^\circ}{30.7 + j13.33}$$

$$\tilde{I}_a = \frac{266 \angle 0^\circ}{33.5 \angle 23.5^\circ} = 7.95 \angle -23.5^\circ \text{ A}$$

$$P_{L1\phi} = |\tilde{I}_a|^2 R_{LY} = (7.95)^2 \left(\frac{80}{3}\right) = 1685 \text{ W}$$

$$Q_{L1\phi} = |\tilde{I}_a|^2 X_{LY} = (7.95)^2 \left(\frac{40}{3}\right) = 843 \text{ VAR}$$

$$S_{L1\phi} = P_{L1\phi} + jQ_{L1\phi} = 1884 \angle 26.6^\circ \text{ VA}$$

Source $S_{3\phi}$
 $3 \left(\frac{460}{\sqrt{3}} \angle 0^\circ\right) (7.95 \angle +23.5^\circ)$
 $= 6334 \angle 23.5^\circ \text{ VA}$

① $S_{L3\phi} = 3S_{L1\phi} = 5652 \angle 26.6^\circ \text{ VA} \quad (5054 + j2531) \text{ VA}$

② $\tilde{V}_{anL} = Z_Y \tilde{I}_a = \left(\frac{80 + j40}{3}\right) (7.95 \angle -23.5^\circ) = (29.8 \angle 26.6^\circ) (7.95 \angle -23.5^\circ)$

$\tilde{V}_{anL} = 237 \angle 3.1^\circ$, $\tilde{V}_{abL} = \sqrt{3} \tilde{V}_{anL} \cdot \frac{1}{\sqrt{3}} = 410 \angle 33.1^\circ \text{ V}$